

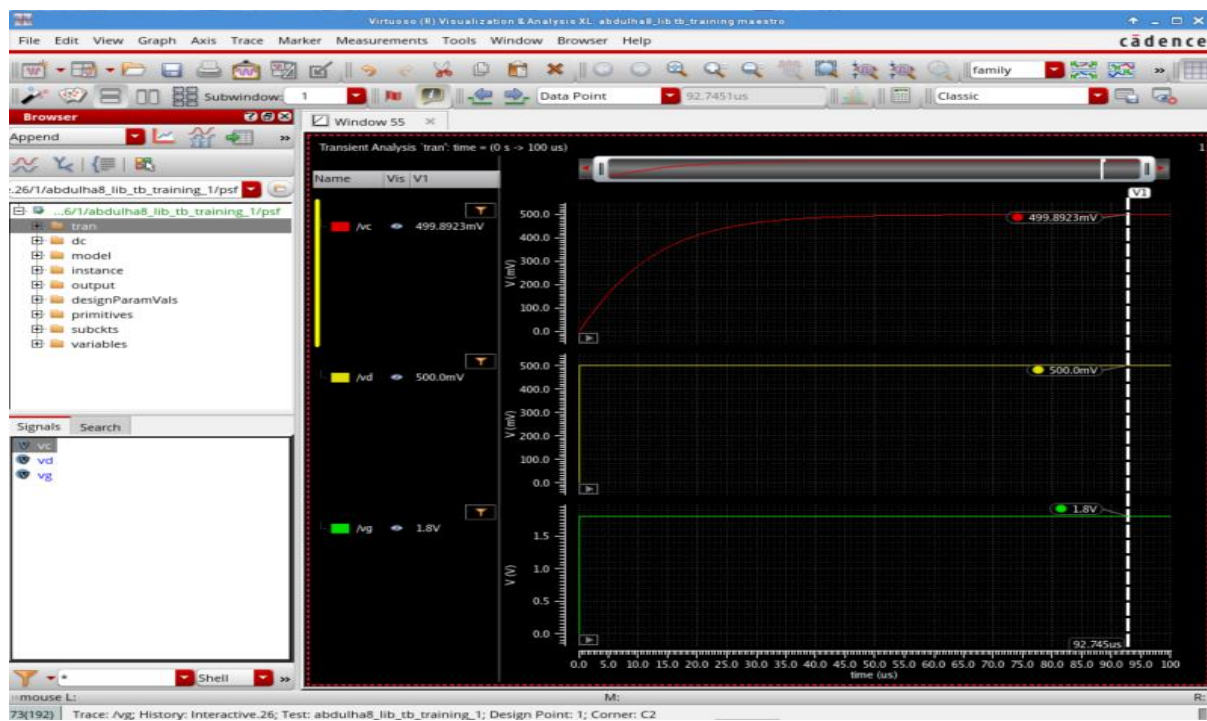
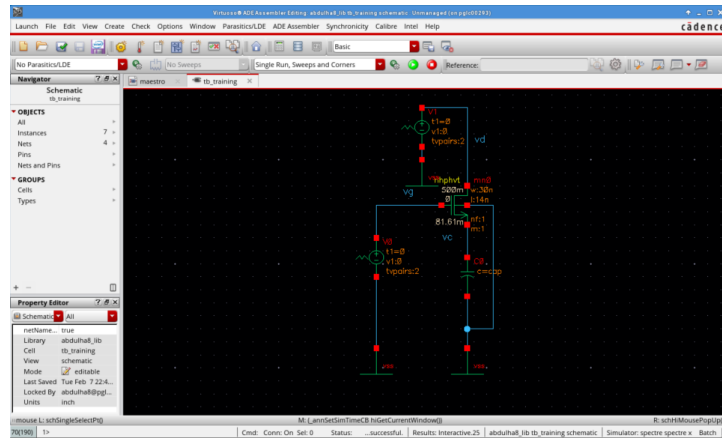
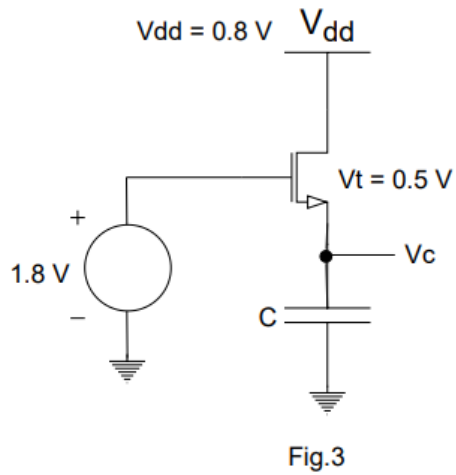
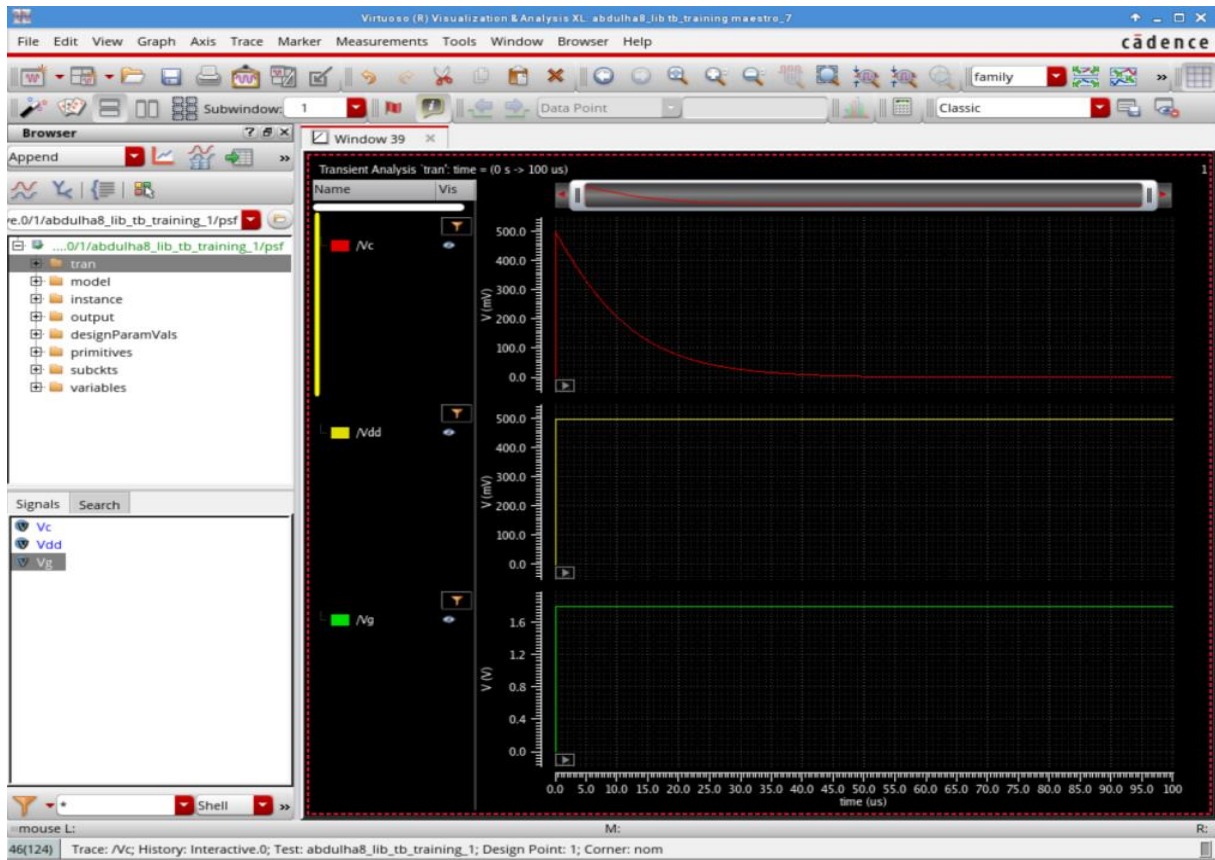


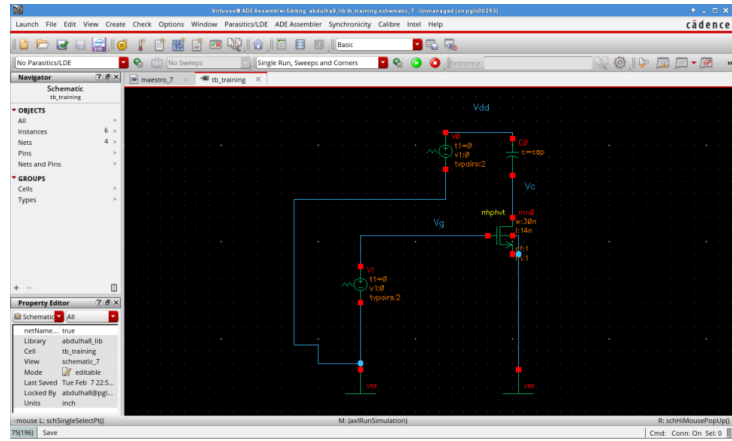MOSFET with Capacitor: 3, 7, 11, 15, 19, 23, 25-30



Cap= 5nF

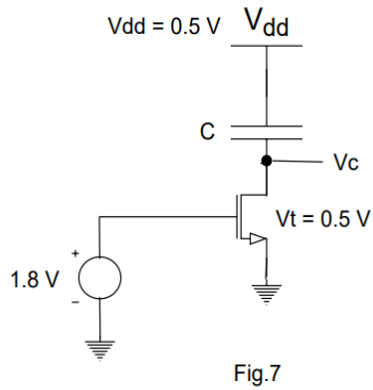Q-7: Initially capacitor C is discharged. Find the value of V_c at steady state. Draw the waveform of V_c vs Time.



Cap= 5nF

Q-11: Initially capacitor C is charged to 1.8 V.
Find the value of V_c at steady state. Draw the waveform of V_c vs Time.


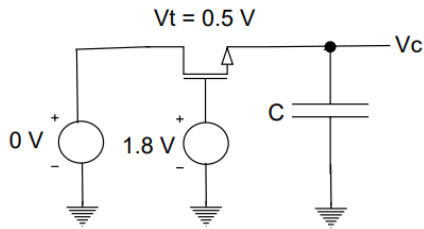
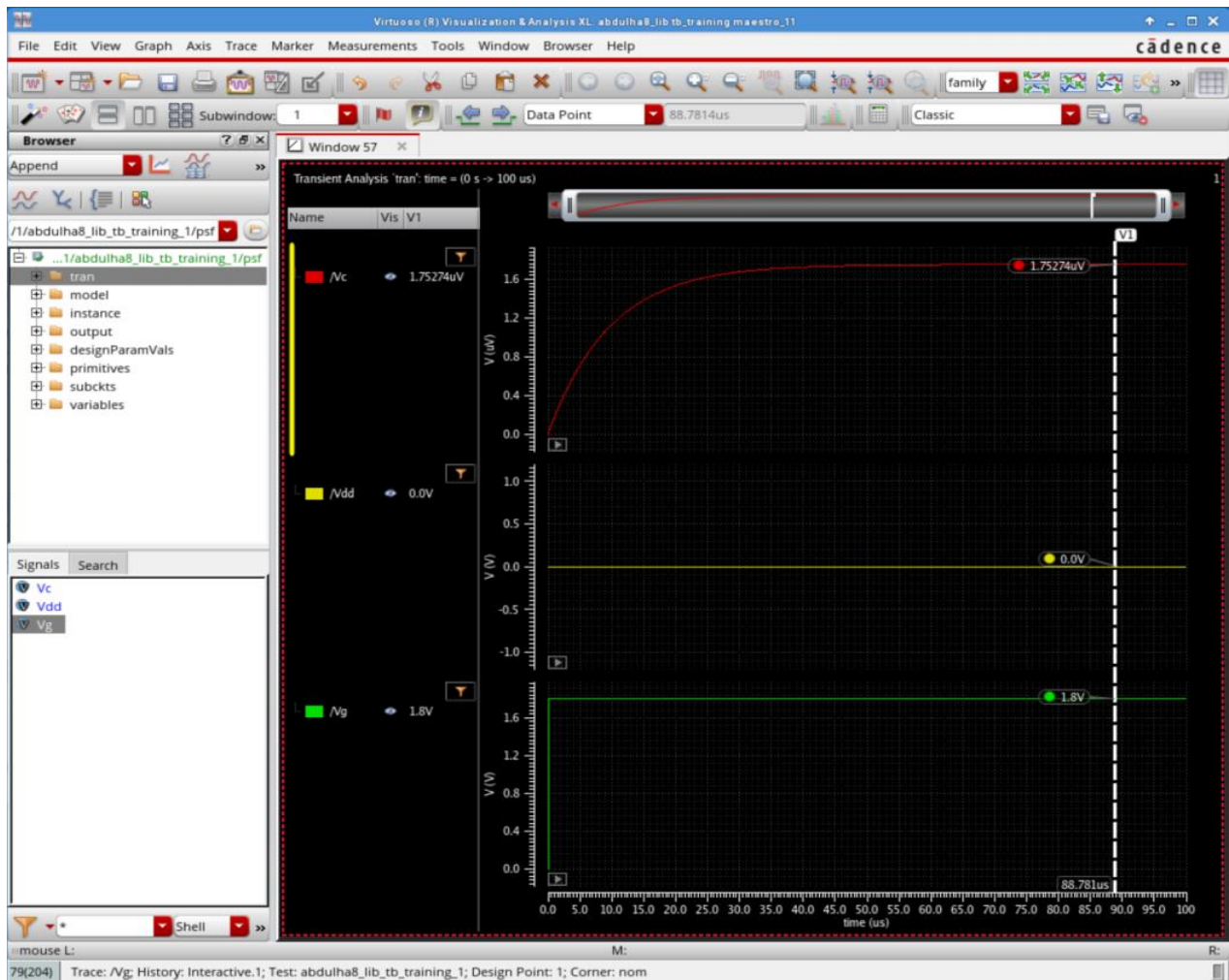


Fig.11

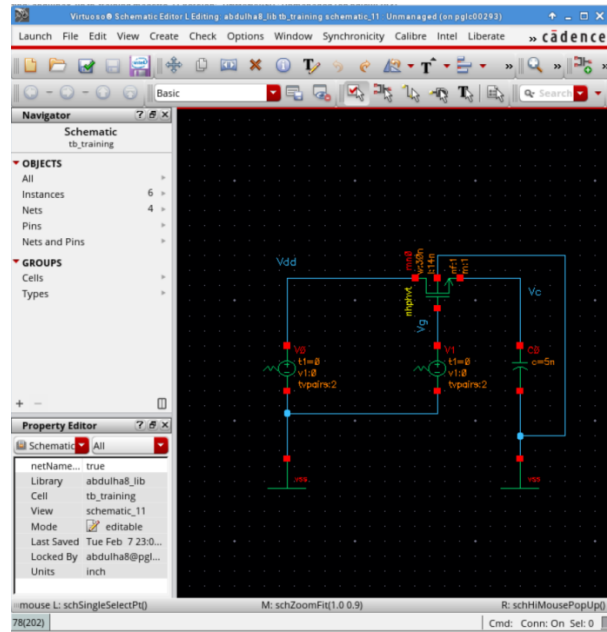

Q-15: Initially capacitor C is discharged. Find the value of V_c at steady state. Draw the waveform of V_c vs Time.


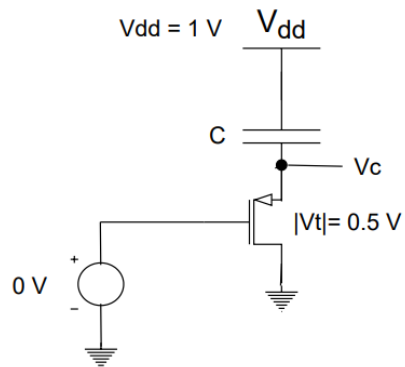
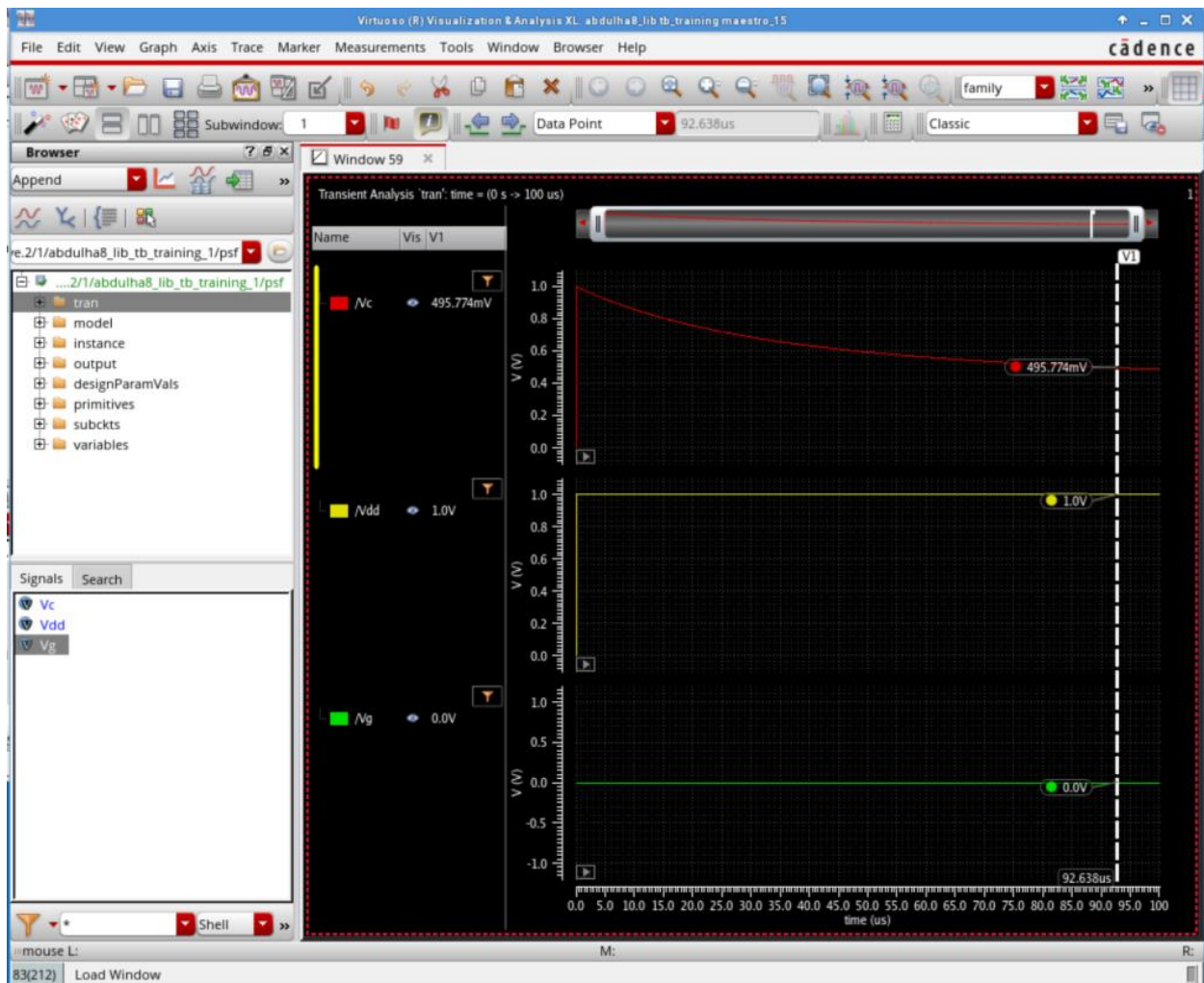


Fig.15

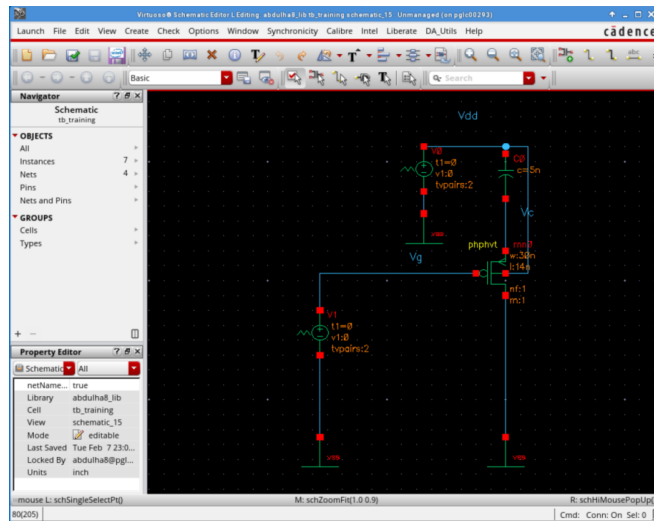

Q-19: Initially capacitor C is discharged. Find the value of V_c at steady state. Draw the waveform of V_c vs Time.


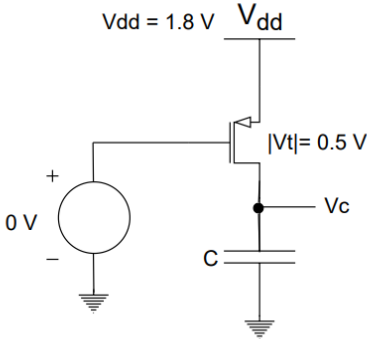
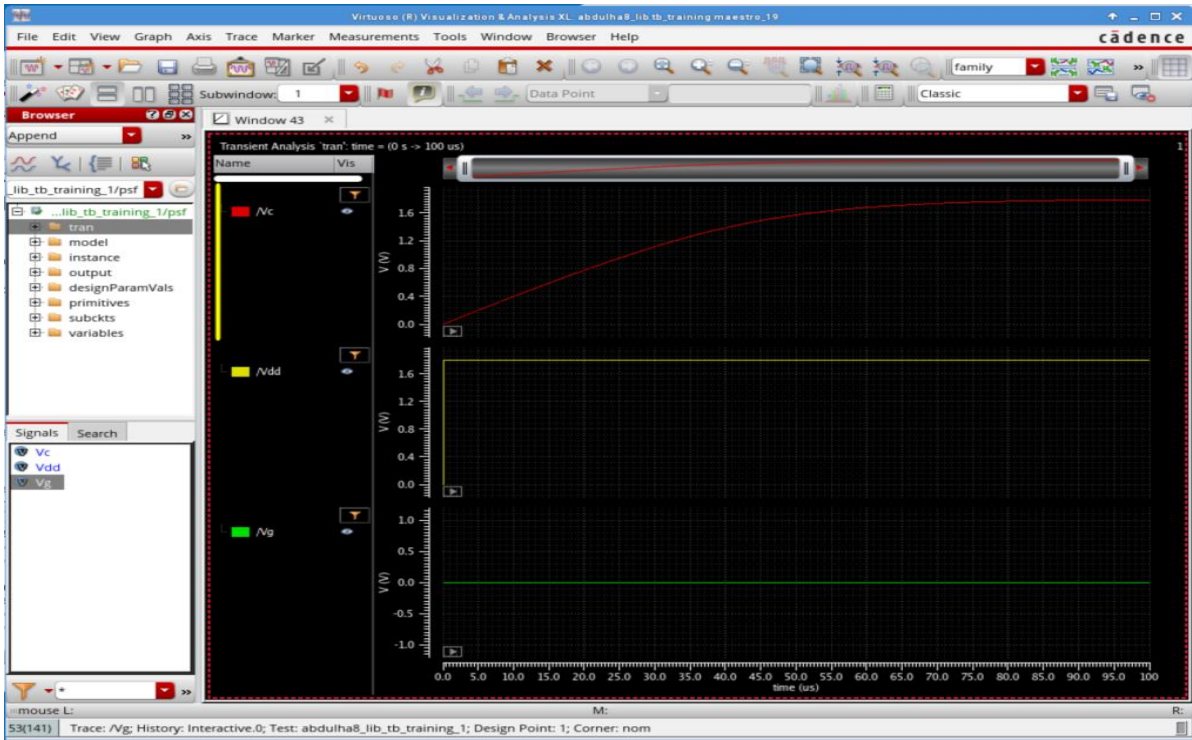


Fig.19

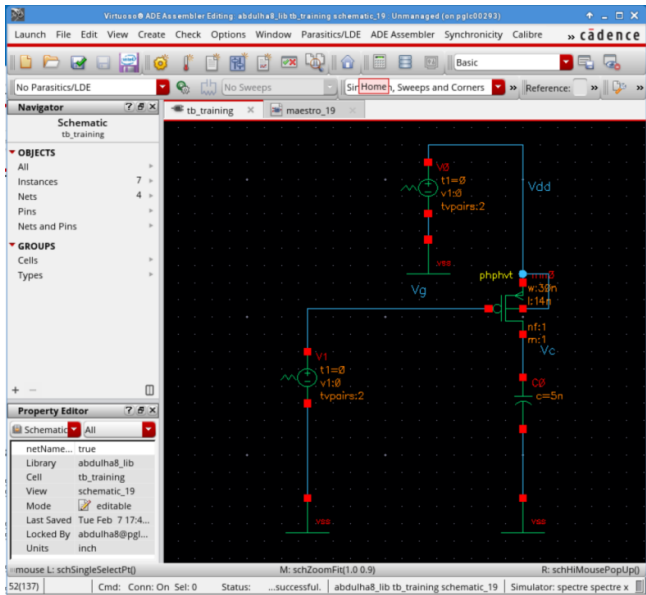

Q-23: Initially capacitor C is charged to 1.8 V. Find the value of V_c at steady state. Draw the waveform of V_c vs Time. Assume for PMOS higher potential terminal is source


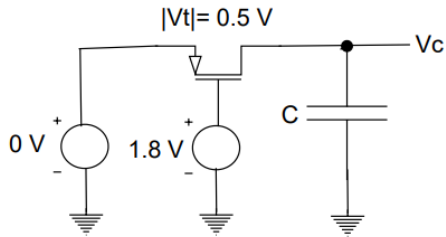
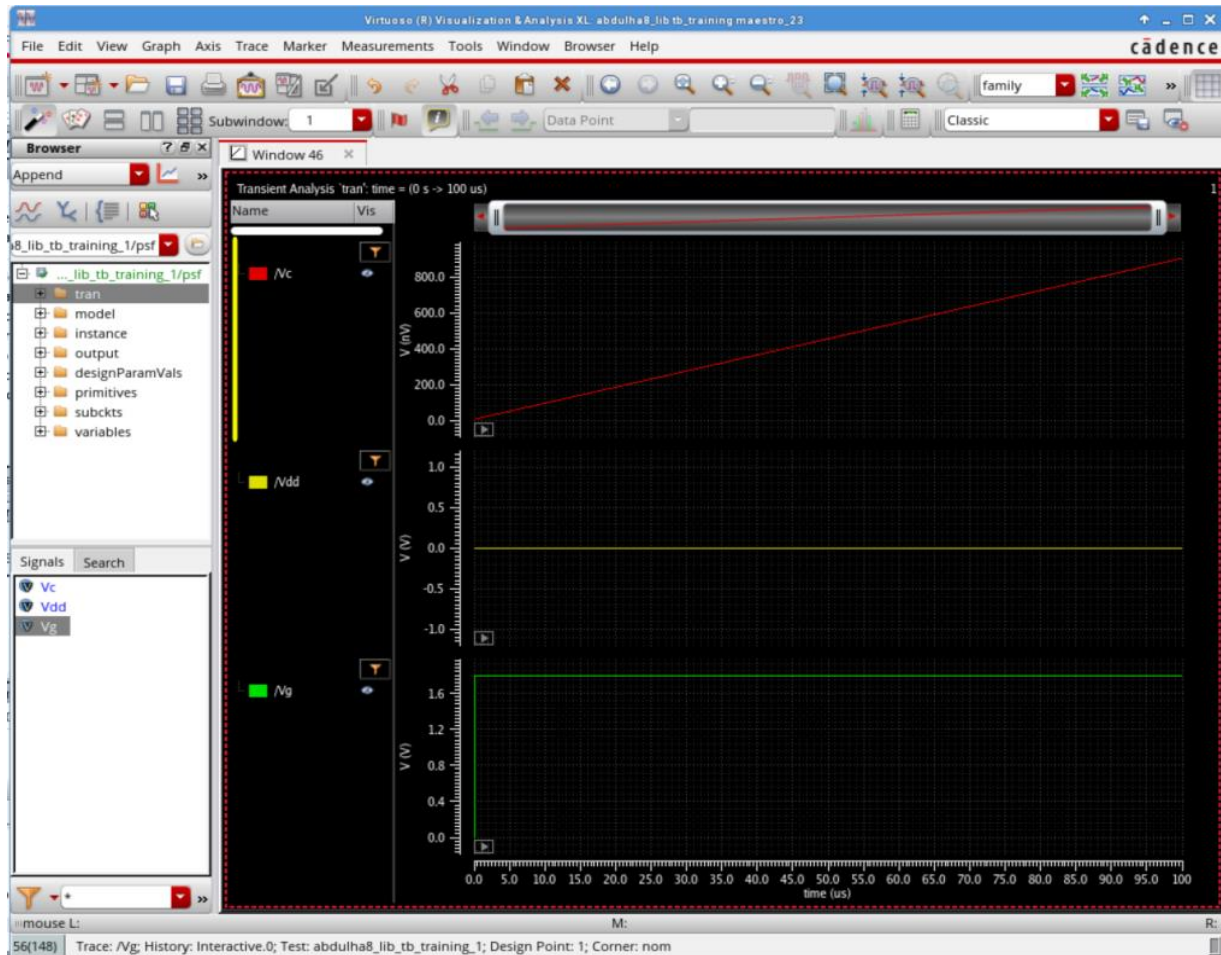


Fig.23

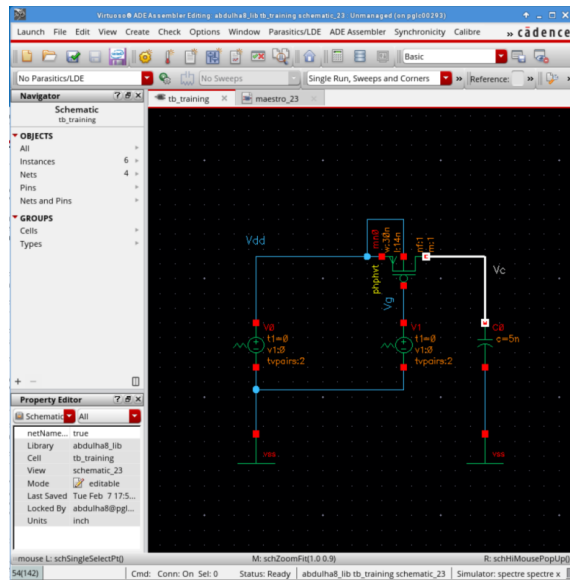

Q-25: Initially capacitor C is discharged. Find the value of V_c and V_A at steady state.


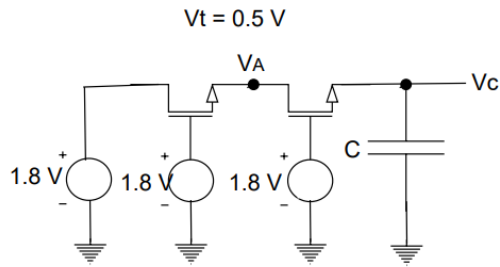
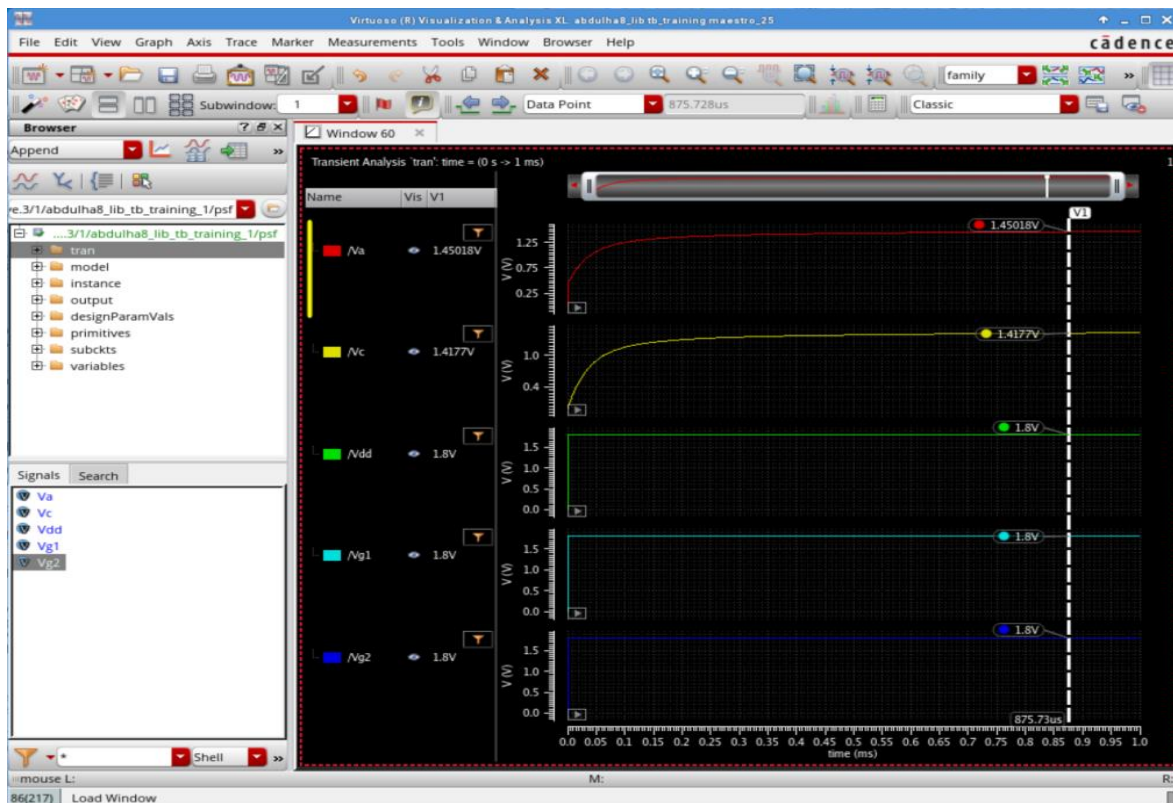


Fig.25

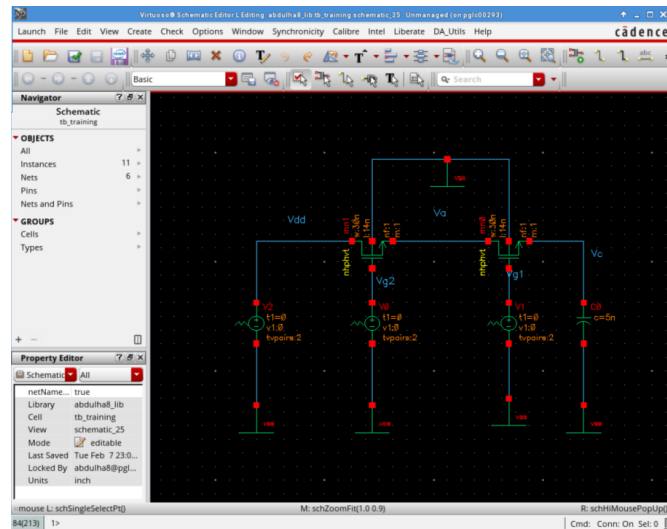

Q-26: Initially capacitor C is discharged. Find the value of V_C and V_A at steady state.


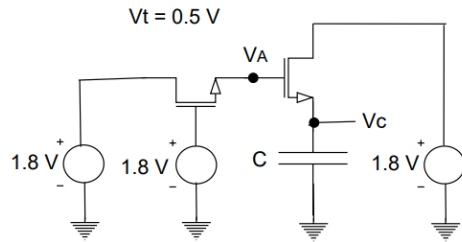
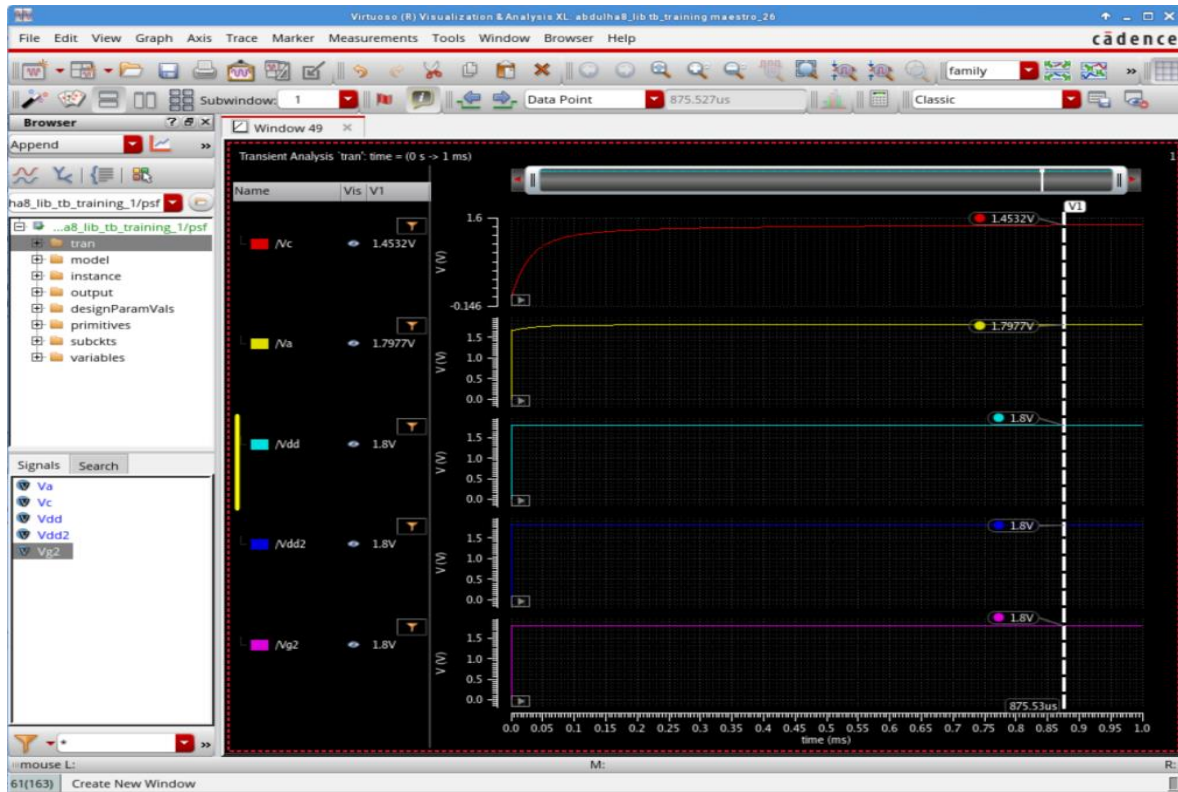


Fig.26

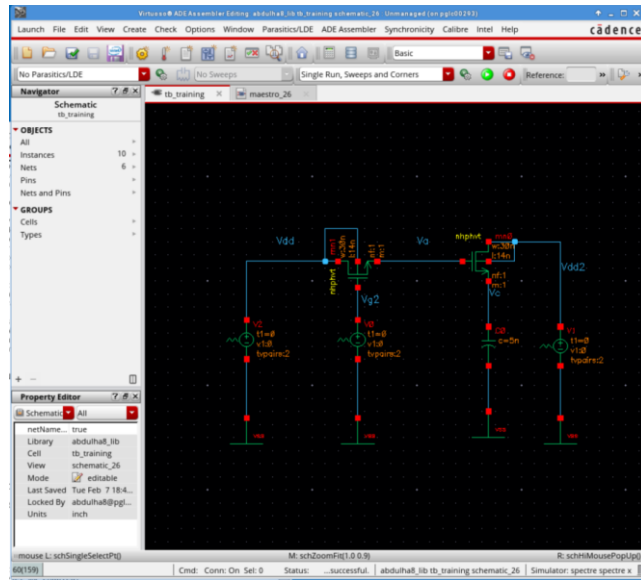

Q-27: Initially capacitor C is discharged. Find the value of V_c and V_A at steady state.


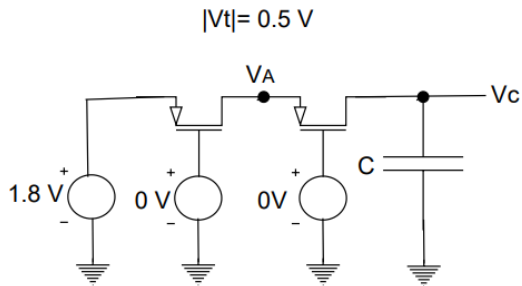
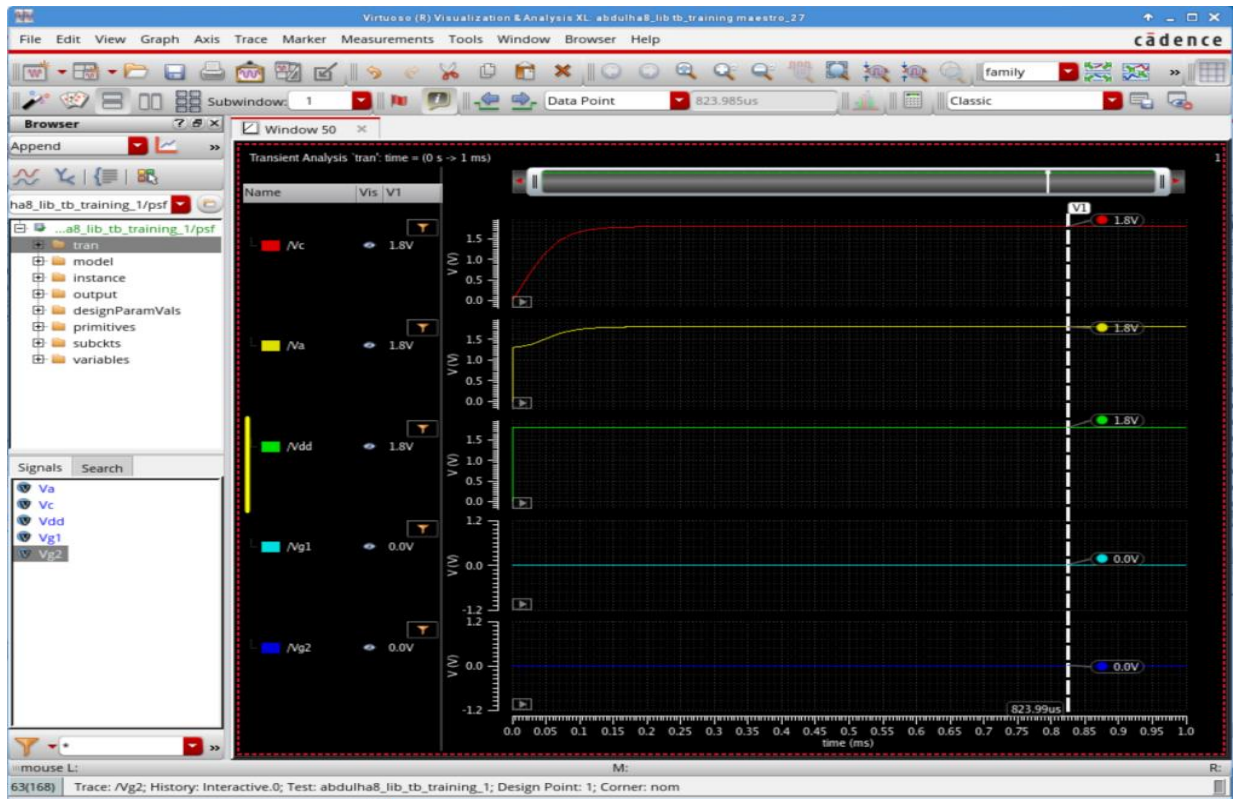


Fig.27

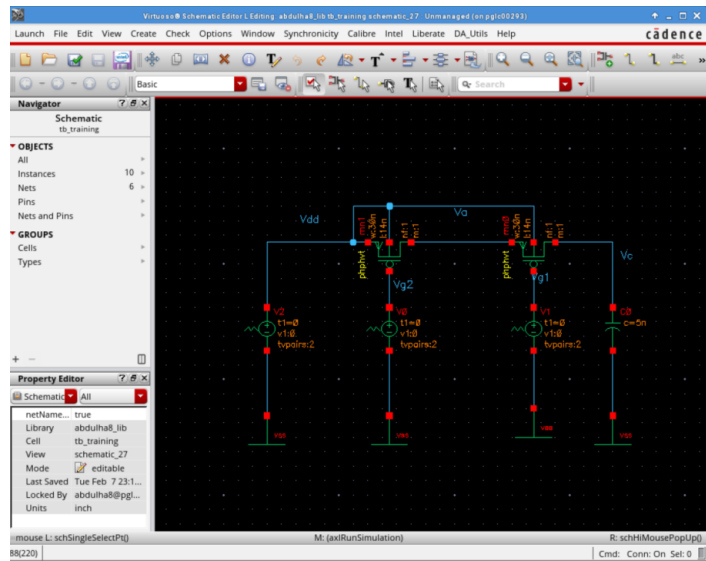

Q-28: Initially capacitor C is discharged. Find the value of V_c and V_A at steady state.


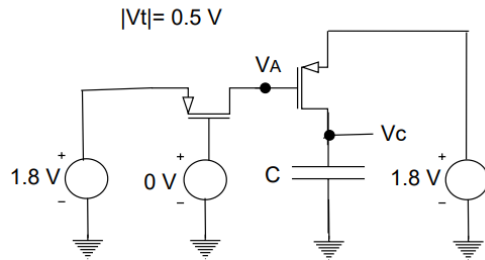
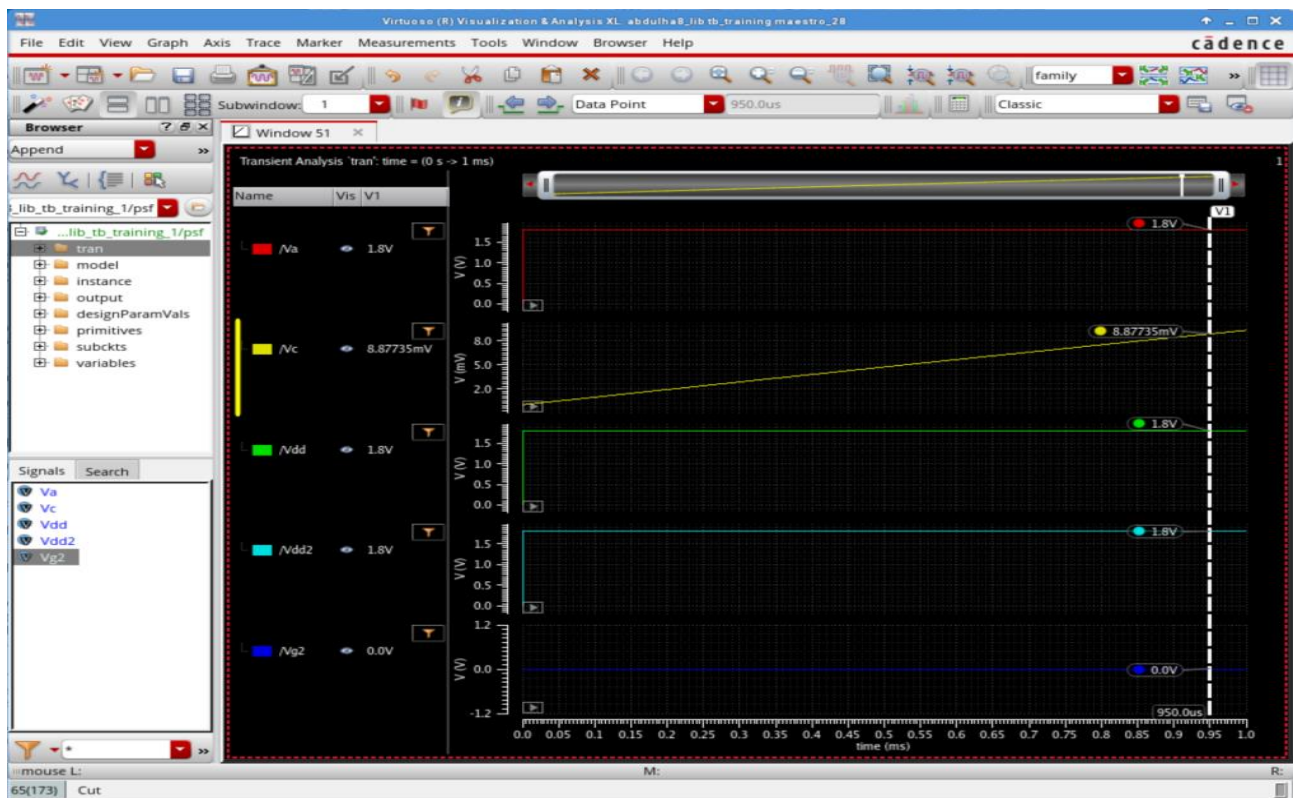


Fig.28

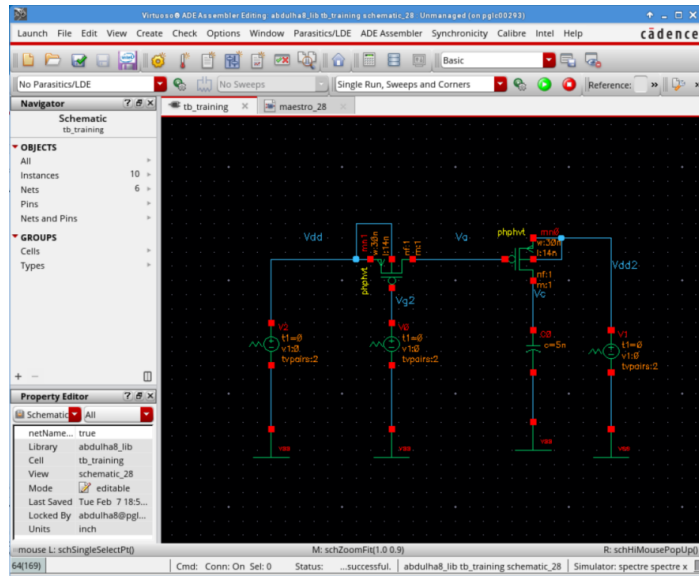

Q-29: Initially capacitor C is fully charged to 1.8 V. Find the value of V1, V2, V3 and V4 at steady state.



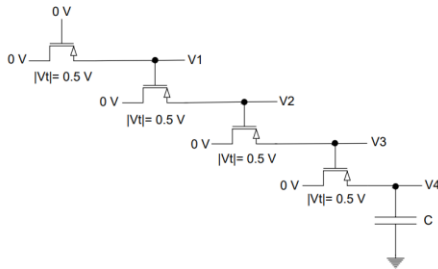


Fig.29

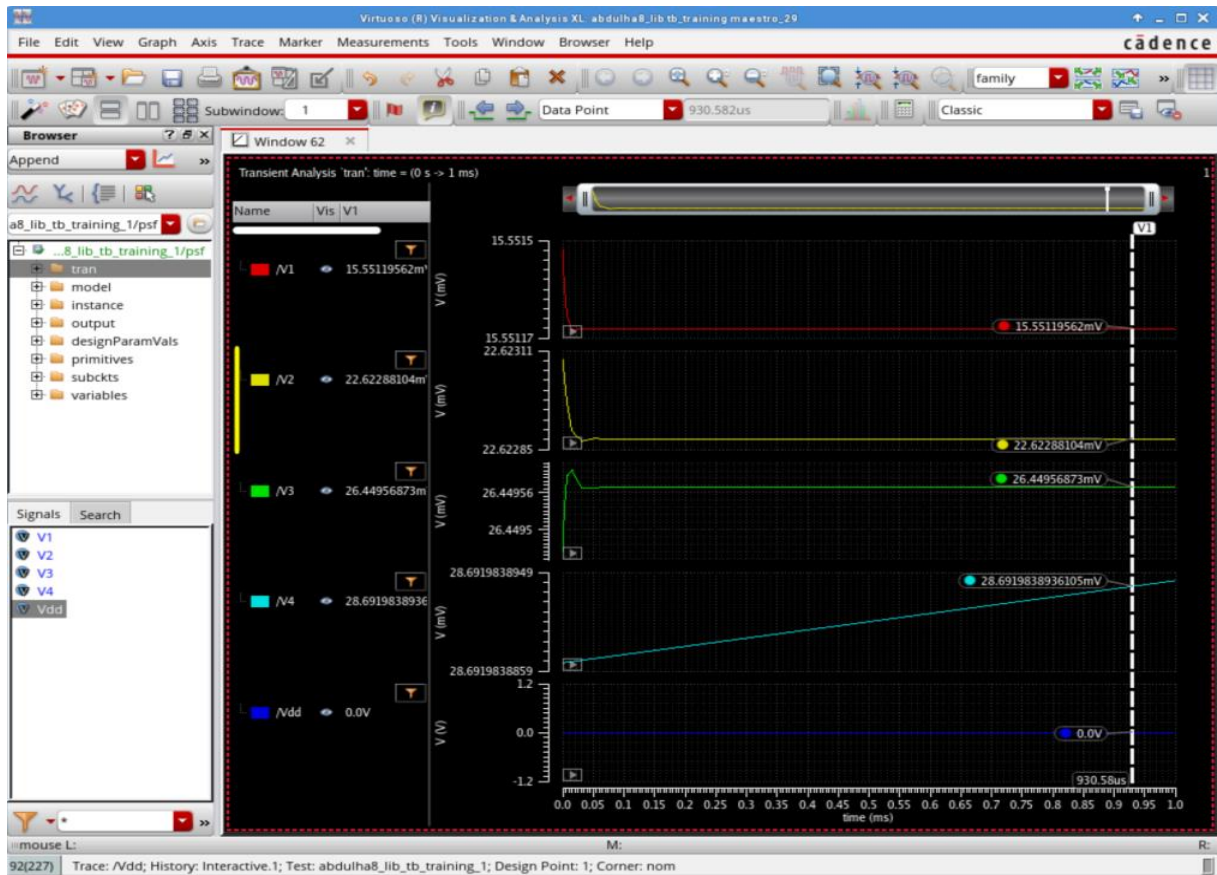

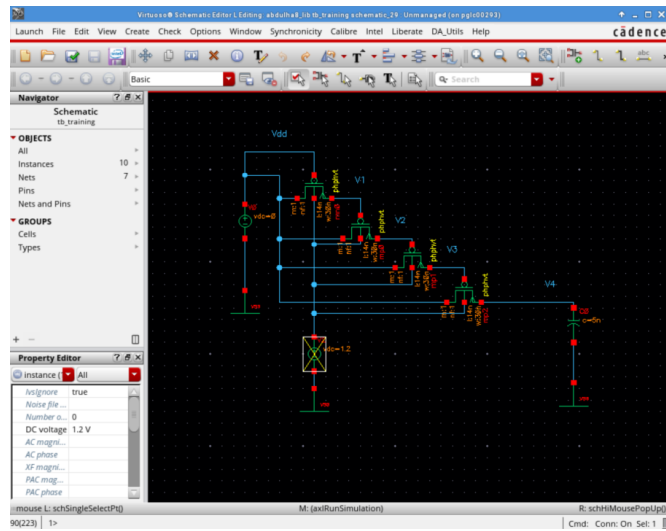Q-30: Initially capacitor C is fully discharged 0V. Find the value of V1, V2, V3 and V4 at steady state. Assume the higher potential side is drain terminal.

